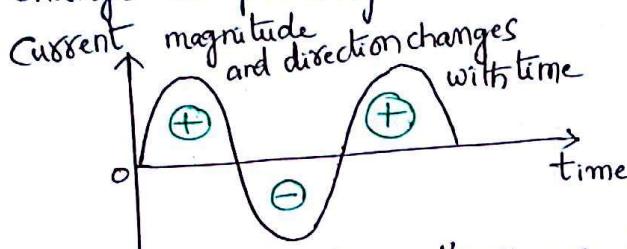


Alternating Quantities


Electrical Supply used for commercial and domestic purpose is of alternating nature.

Alternating Current : (A.C) An alternating current wave form is defined as the current that fluctuates with time periodically, with change in polarity and direction.



In alternating waveform there are two half cycles, one positive and other negative. These two half cycles make one cycle. Current increases in magnitude, in one particular direction, attains maximum and starts decreasing, passing through zero it increases in opposite direction and behaves similarly.

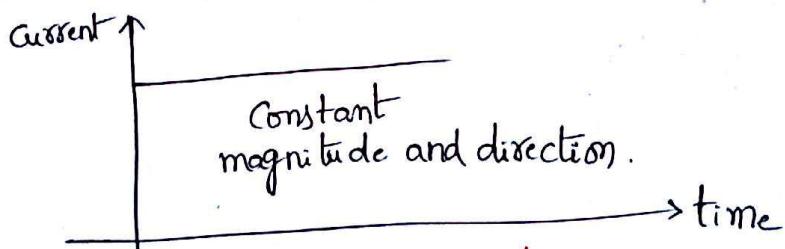Direct Current : (D.C) The d.c supply has constant magnitude with respect to time.




Standard Definitions Related to Alternating Quantity

1. Cycle :- The complete positive and negative portion of the wave is one cycle of the Sine wave

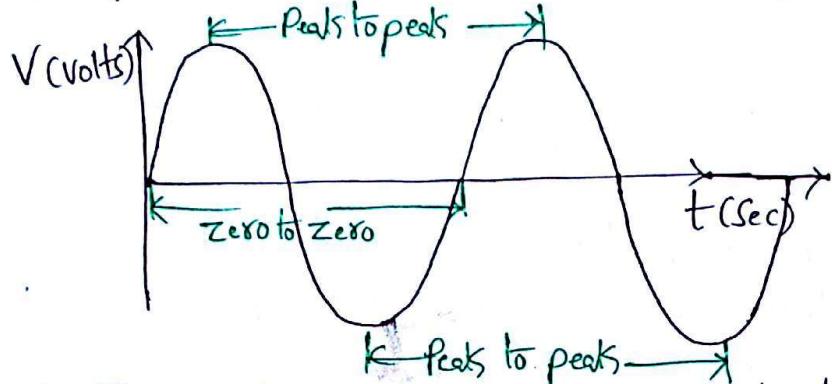2. Time Period :- The time taken by an alternating quantity to complete its one cycle is known as time period denoted by T seconds.

After every ' T ' seconds, the cycle of an alternating quantity repeats. So it is called **Periodic Wave**.

The period can be measured in the following different ways




1. From Zero crossing of one cycle to Zero crossing of the next cycle.
2. From positive peaks of cycle to positive peaks of the next cycle
3. From negative peaks of one cycle to negative peak of the next cycle.

3. Frequency :- (f) The number of cycles completed by an alternating quantity per second is known as its frequency. It is denoted by f and it is measured in Cycles/second (or) Hertz (Hz).

As time period T is time for one cycle i.e. seconds/cycle and frequency is cycles/second

So
$$f = \frac{1}{T} \text{ Hz}$$

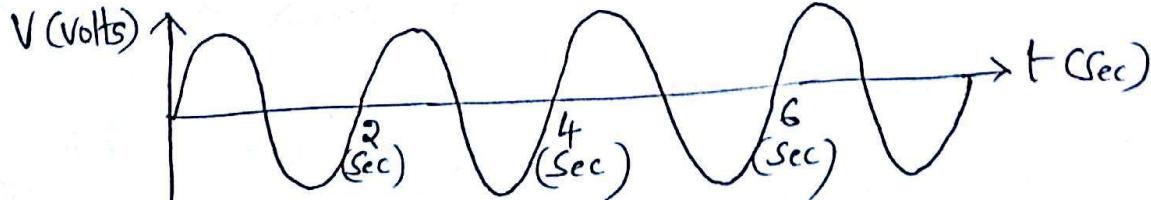I) Find the time period and frequency for the Sine wave shown below?




The Sine wave takes two seconds to complete one period in each cycle.

$$T = 2 \text{ sec}$$

$$f = \frac{1}{T} = \frac{1}{2} = 0.5 \text{ Hz.}$$

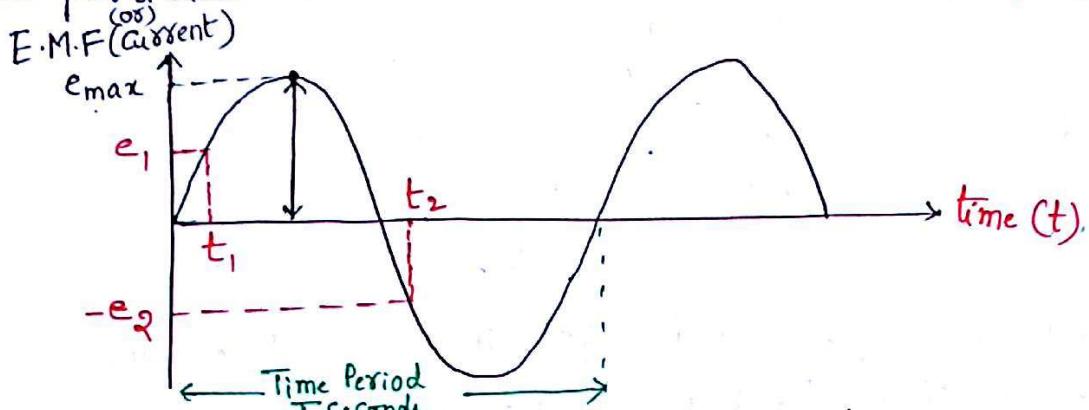4. Instantaneous Value: The value of an alternating quantity at a particular instant is known as its instantaneous value. (2)



where e_1 and $-e_2$ are the instantaneous values of an alternating e.m.f (or) Voltage at the instants t_1 and t_2 respectively.

5. Amplitude:- The maximum value attained by an alternating quantity during positive (or) negative half cycle is called its amplitude. It is denoted as E_m (or) I_m .

Thus E_m is called peak value of the voltage while I_m is called peak value of the current.

So the amplitude is also called peak value (or) maximum value of an alternating quantity.

6. Peaks to Peaks Value:- The value of an alternating quantity from its positive peaks to negative peaks is called its peak to peak value. It is denoted as I_{p-p} (or) V_{p-p}

$$\text{Amplitude} = \frac{\text{Peaks to peaks Value}}{2}$$


Angular relation of a Sine wave :-

A Sine wave can be measured along the X-axis on a time base which is frequency dependent.

A Sinewave can also be expressed in terms of an angular measurement. This angular measurement is expressed in degrees (or) radians.

$$1 \text{ radian} = 57.3^\circ, \text{ in a } 360^\circ \text{ revolution.}$$

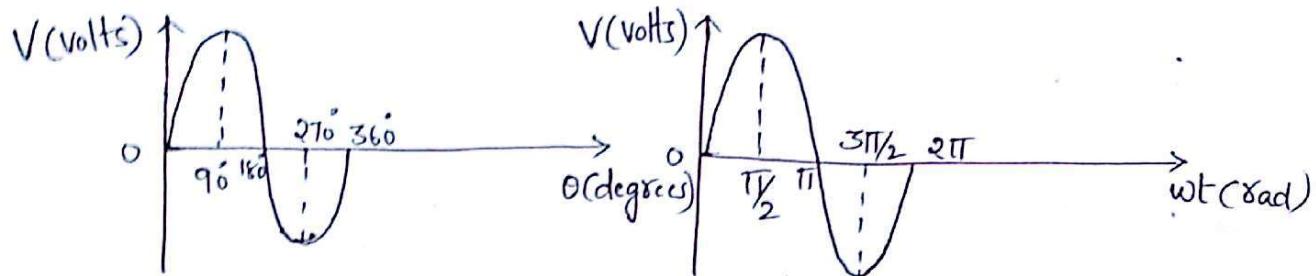The angular measurement of a Sine wave is based on 360° (or) 2π radians for a complete cycle shown below.



A Sine wave completes a half-cycle in 180° (or) π radians, a quarter cycle in 90° (or) $\pi/2$ radians, and so on.

where ω = Angular frequency

$$\omega = 2\pi f \quad \text{units: radians/second}$$

$$(or) \omega = \frac{2\pi}{T}$$

$$\theta = \omega t \quad (\text{radians}) \quad \theta = 2\pi ft \quad (\text{radians}).$$

The Sinewave equation :-

As the standard wave form of an alternating quantity is purely sinusoidal, the equation of an alternating Voltage can be expressed as

$$V(t) = V_m \sin \omega t \quad (or) \quad e = E_m \sin \omega t$$

Where V_m = Amplitude (or) maximum (or) peak value of the Voltage

Similarly equation of an alternating Current can be expressed as

$$(or) i = I_m \sin \omega t$$

$$i(t) = I_m \sin 2\pi ft$$

I_m = Amplitude (or) maximum (or) peaks value of the current

i = Instantaneous Value of an alternating current.


2) A Sinusoidal wave of frequency 50 Hz has its maximum value of 9.2 Amps. What will be its value at (a) 0.002 sec after the wave passes through zero in positive direction (b) 0.0045 sec after the wave passes through positive maximum. Show the values of current in a neat sketch of the waveform?

Sol.

$$\text{Given } I_m = 9.2 \text{ Amps}$$

$$f = 50 \text{ Hz}$$

$$i = I_m \sin 2\pi f t$$

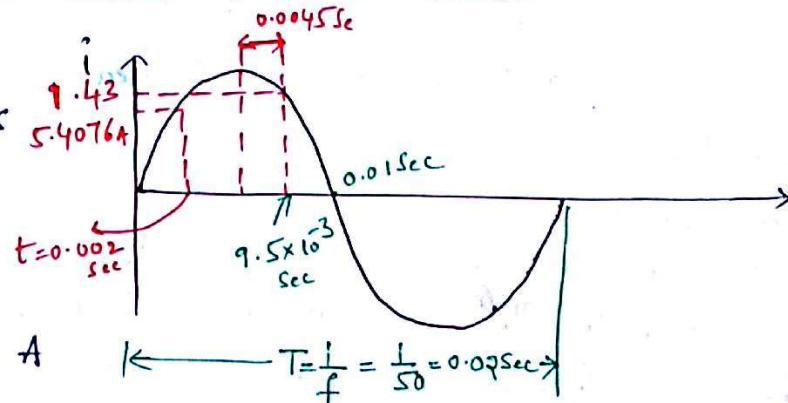

$$i(t) = 9.2 \sin 100\pi t \text{ A} \quad \leftarrow T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ sec}$$

a) at $t = 0.002 \text{ sec}$

$$i(0.002) = 9.2 \sin(100\pi \times 0.002) = 5.4076 \text{ A}$$

use sin in radians mode

(b) at $t = 0.0045 \text{ sec}$ after positive maximum

$$\text{i.e. } T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ sec}$$

So positive maximum occurs at $T/4 = \frac{0.02}{4} = 0.005$
after this 0.0045 sec means value of i at $= 5 \times 10^{-3} \text{ sec}$


$$t = 5 \times 10^{-3} + 0.0045 = 0.0095 \text{ sec}$$

$$i(0.0095) = 9.2 \sin(2\pi \times 50 \times 0.0095) = 1.4391 \text{ A}$$

Root mean Square Value (or) Effective Value :-

Root mean square values are used to analyse the effect of an alternating quantity.

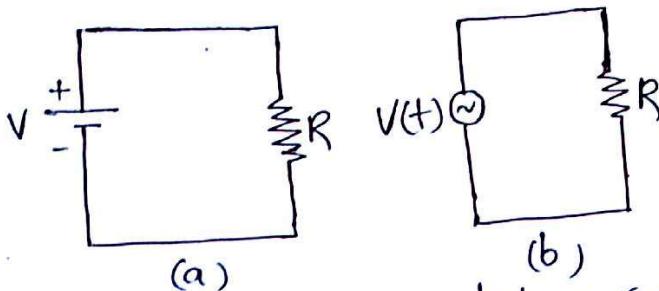The root mean square value of a sine wave is a measure of the heating effect of the wave.



when a resistor is connected across a dc voltage source as shown in fig(a), a certain amount of heat is produced in the resistor in a given time.

A similar resistor is connected across an ac voltage source for the same time as shown in fig(b). The value of the ac voltage is adjusted such that the same amount of heat is produced in the resistor as in the case of the dc source. This value is called the V_{rms} value.

The V_{rms} value of a sine wave is equal to the dc voltage that produces the same heating effect.

The V_{rms} value of any function with period T has an effective value given by

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt}$$

Consider a function $V(t) = V_p \sin \omega t$

For Sine wave $T = 2\pi$

$$\text{The } V_{rms} \text{ value, } V_{rms} = \sqrt{\frac{1}{T} \int_0^T (V_p \sin \omega t)^2 d(\omega t)}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_p^2 \sin^2 \omega t d(\omega t)}$$

$$= \sqrt{\frac{V_p^2}{2\pi} \int_0^{2\pi} \left[1 - \frac{\cos 2\omega t}{2} \right] d(\omega t)}$$

$$= \sqrt{\frac{V_p^2}{2\pi} \left[\frac{1}{2}(2\pi - 0) - \frac{1}{2} (\sin 2\omega t) \Big|_0^{2\pi} \right]}$$

$$= \sqrt{\frac{V_p^2}{2\pi} [2\pi - 0]} = \sqrt{\frac{V_p^2}{2\pi} \times 2\pi} = \frac{V_p}{\sqrt{2}}$$

$$= \sqrt{\frac{V_p^2}{2\pi} \times 2\pi} = \frac{V_p}{\sqrt{2}}$$

$$\therefore V_{\text{rms}} = \frac{V_p}{\sqrt{2}} = 0.707 V_p \quad (4)$$

If the function consists of a number of sinusoidal terms, that is

$$v(t) = V_0 + (V_1 \cos \omega t + V_2 \cos 2\omega t + \dots) + (V_1 \sin \omega t + V_2 \sin 2\omega t + \dots)$$

The rms (or) effective value is given by

$$V_{\text{rms}} = \sqrt{V_0^2 + \frac{1}{2}(V_1^2 + V_2^2 + \dots) + \frac{1}{2}(V_1^2 + V_2^2 + \dots)}$$

- 3) A wire is carrying a direct current of $20A$ and a sinusoidal alternating current of peaks value $20A$. find the rms value of the resultant current in the wire?

The rms value of the combined wave

$$= \sqrt{20^2 + \frac{20^2}{2}}$$

$$= \sqrt{400 + 200} = \sqrt{600} = 24.5A$$

Note:- The rms value of the sinusoidal alternating voltage (or) current is 0.707 times the maximum (or) peaks value of that alternating current (or) Voltage.

Average Value:- The average value of an alternating quantity is defined as that value which is obtained by averaging all the instantaneous values over a period of half cycle.

The average value of any function with period T is given by

$$V_{\text{avg}} = \frac{1}{T} \int_0^T v(t) dt$$

Consider a function $v(t) = V_m \sin \omega t$

$$V_{\text{avg}} = \frac{1}{T} \int_0^T V_m \sin \omega t d(\omega t)$$

$$= \frac{V_m}{\omega T} \left[-\cos \omega t \right]_0^{T\omega} = \frac{V_m}{\omega T} [-\cos \omega T + \cos 0] \\ = \frac{2V_m}{\omega T} = 0.637 V_m$$

Crest (or) Peaks Factor (k_p)

The peaks factor of an alternating quantity is defined as ratio of maximum value to the r.m.s value.

$$k_p = \frac{\text{Maximum Value}}{\text{r.m.s Value}}$$

The peaks factor for Sinusoidally Varying, alternating Currents and Voltages can be obtained as,

$$k_p = \frac{V_m}{0.707 V_m} = 1.414$$

Form factor:-


The form factor of an alternating quantity is defined as the ratio of r.m.s Value to the average Value.

$$k_f = \frac{\text{r.m.s Value}}{\text{Average Value}}$$

for Sinusoidal alternating Currents (or) Voltages

$$k_f = \frac{0.707 I_m}{0.637 I_m} = 1.11$$

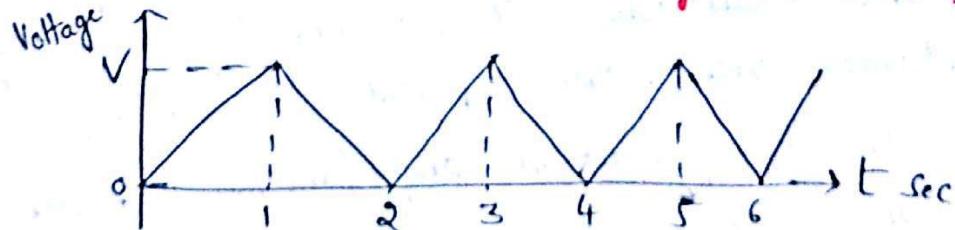4) Find the form factor for the following wave form?



Sol

The time period of the wave-form $T = 1 \text{ sec.}$

$$\text{From } 0 \text{ to } 1, \text{ slope} = \frac{V-0}{1-0} = V, \text{ i.e. } V(t) = Vt \quad (y = mx + c)$$

$$\text{1 to } 2, \text{ slope} = \frac{0-V}{2-1} = -V$$

$$\therefore V(t) = -Vt + C$$

$$\text{at } t=2, V(t)=0$$

$$0 = -2V + C \Rightarrow C = 2V$$


$$\therefore V(t) = -Vt + 2V = V[2-t] \quad \text{from } 1 \text{ to } 2$$

$$\begin{aligned}
 \text{Average Value} &= \frac{\text{Area under the curve}}{\text{Base}} = \frac{\int_0^2 v(t) dt}{2} \quad (5) \\
 &= \frac{1}{2} \left[\int_0^1 v(t) dt + \int_1^2 v(t) dt \right] \\
 &= \frac{1}{2} \left[\int_0^1 vt dt + \int_1^2 v(2-t) dt \right] \\
 &= \frac{V}{2} \left[\left(\frac{t^2}{2}\right)_0^1 + \left(2t - \frac{t^2}{2}\right)_1^2 \right] \\
 &= \frac{V}{2} \left[\frac{1}{2} + \left[(4 - \frac{4}{2}) - (2 - \frac{1}{2}) \right] \right] \\
 &= \frac{V}{2} \left[\frac{1}{2} + 2 - \frac{3}{2} \right] = \frac{V}{2} \left[\frac{1}{2} + \frac{1}{2} \right] = \frac{V}{2}
 \end{aligned}$$

$$\begin{aligned}
 \text{Rms Value} &= \sqrt{\frac{1}{2} \int_0^2 v(t)^2 dt} \\
 &= \sqrt{\frac{1}{2} \left[\int_0^1 (vt)^2 dt + \int_1^2 (v(2-t))^2 dt \right]} \\
 &= \frac{1}{\sqrt{2}} \sqrt{V^2 \left[\left(\frac{t^3}{3}\right)_0^1 + \int_1^2 (4+t^2-4t) dt \right]} \\
 &= \frac{1}{\sqrt{2}} \sqrt{V^2 \left[\frac{1}{3} + \left[4t + \frac{t^3}{3} - \frac{4t^2}{2} \right]_1^2 \right]} \\
 &= \frac{1}{\sqrt{2}} \sqrt{V^2 \left[\left(\frac{1}{3}\right) + (4 \times 2 + \frac{8}{3} - 2 \times 4) - \left(\frac{4+1/3-2}{3}\right) \right]} \\
 &= \frac{V}{\sqrt{2}} \sqrt{\left(\frac{1}{3} + \frac{8}{3} - \frac{7}{3}\right)} = \frac{V}{\sqrt{2}} \sqrt{\frac{2}{3}} = \frac{V}{\sqrt{3}}
 \end{aligned}$$

$$\text{Formfactor} = \frac{\text{R.m.s Value}}{\text{Avg Value}} = \frac{0.5773V}{0.5V} = 1.1546$$

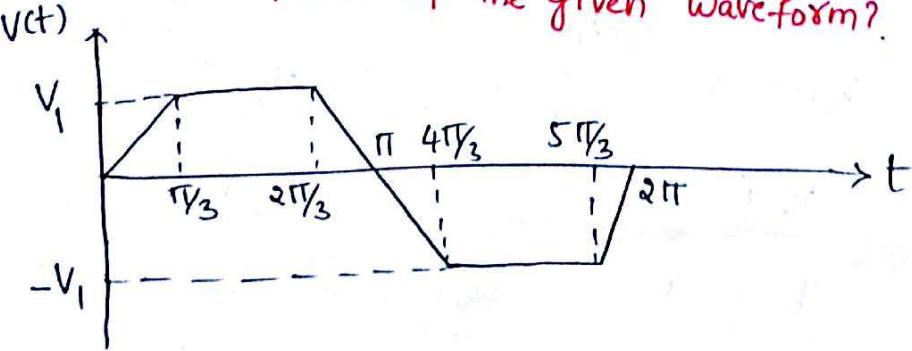5) Find the formfactor of the given waveform?



Time period $T = 2\pi$

Hint: For symmetrical wave-form find R.m.s value by considering half wave that will be equals to R.m.s value for full wave.

So consider $T = \pi$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$

$$= \sqrt{\frac{1}{\pi} \int_0^\pi V^2(t) dt}$$

$$= \sqrt{\frac{1}{\pi} \left[\int_0^{\pi/3} V_1^2(t) dt + \int_{\pi/3}^{2\pi/3} V_2^2(t) dt + \int_{2\pi/3}^\pi V_3^2(t) dt \right]}$$

$\Rightarrow V_1(t)$ from $(0, 0)$ to $(\pi/3, V_1)$

$$y - y_1 = \left(\frac{y_2 - y_1}{x_2 - x_1} \right) (x - x_1)$$

$$\begin{aligned} y &= V_1(t) \\ x &= t \end{aligned} \quad (V_1(t) - 0) = \left(\frac{V_1 - 0}{\pi/3 - 0} \right) (t - 0)$$

$$\boxed{V_1(t) = \frac{3V_1 t}{\pi}}$$

$$\begin{aligned} \Rightarrow \int_0^{\pi/3} \left(\frac{3V_1 t}{\pi} \right)^2 dt &= \frac{9V_1^2}{\pi^2} \left(\frac{t^3}{3} \right) \Big|_0^{\pi/3} \\ &= \frac{9V_1^2}{\pi^2} \left(\frac{\pi^3}{27 \times 3} \right) = \boxed{\frac{V_1^2 \pi}{9}} \rightarrow ① \end{aligned}$$

$\Rightarrow V_2(t)$ if it is parallel to x-axis

$$\text{so } V_2(t) = V_1$$

$$\Rightarrow \int_{\pi/3}^{2\pi/3} V_1^2 dt = V_1^2 \left(\frac{2\pi}{3} - \frac{\pi}{3} \right) = \boxed{\frac{V_1^2 \pi}{3}} \rightarrow ②$$

$\Rightarrow V_3(t)$ from $(2\pi/3, V_1)$ to $(\pi, 0)$

$$y - y_1 = \left(\frac{y_2 - y_1}{x_2 - x_1} \right) (x - x_1)$$

$$V_3(t) - V_1 = \left(\frac{0 - V_1}{\pi - 2\pi/3} \right) (t - 2\pi/3)$$

$$V_3(t) - V_1 = -\frac{3V_1}{\pi} (t - 2\pi/3)$$

$$V_3(t) - V_1 = -\frac{3V_1 t}{\pi} + \frac{3V_1}{\pi} \times \frac{2\pi}{3}$$

$$V_3(t) = -\frac{3V_1 t}{\pi} + 2V_1 + V_1 = -\frac{3V_1 t}{\pi} + 3V_1$$

$$V_3(t) = 3V_1 (1 - \frac{t}{\pi})$$

$$\begin{aligned}
 & \Rightarrow \int_{\frac{\pi}{2}V_3}^{\pi} \left(3V_1 - \frac{3V_1 t}{\pi} \right) dt \quad (6) \\
 & \Rightarrow \int_{\frac{\pi}{2}V_3}^{\pi} \left[\frac{9V_1^2 t^2}{\pi^2} - \frac{18V_1^2 t}{\pi} + 9V_1^2 \right] dt \\
 & \Rightarrow 9V_1^2 \left[\frac{1}{\pi^2} \left(\frac{t^3}{3} \right) - \frac{2}{\pi} \left(\frac{t^2}{2} \right) + t \right] \Big|_{\frac{\pi}{2}V_3}^{\pi} \\
 & \Rightarrow 9V_1^2 \left[\left(\frac{1}{\pi^2} \left(\frac{\pi^3}{3} \right) - \frac{2}{\pi} \times \frac{\pi^2}{2} + \pi \right) - \left(\frac{1}{\pi^2} \frac{8\pi^3}{27V_3} - \frac{2}{\pi} \left(\frac{4\pi^2}{9V_2} \right) + \frac{2\pi}{3} \right) \right] \\
 & \Rightarrow 9V_1^2 \left(\left(\frac{\pi}{3} - \frac{8\pi}{81} + \pi \right) - \left(\frac{8\pi}{27V_3} - \frac{4\pi}{9} + \frac{2\pi}{3} \right) \right) \\
 & 9V_1^2 \left[\frac{\pi}{3} - \frac{8\pi}{81} + \frac{4\pi}{9} - \frac{2\pi}{3} \right] \\
 & \Rightarrow 9V_1^2 \left[\frac{27\pi - 8\pi + 36\pi - 54\pi}{81} \right] \\
 & = V_1^2 \frac{(63\pi - 62\pi)}{9} = \boxed{\frac{V_1^2 \pi}{9}} \rightarrow (2) \\
 V_{rms} &= \sqrt{\frac{1}{\pi} \left[(1) + (2) + (3) \right]} \\
 &= \sqrt{\frac{1}{\pi} \left(\frac{V_1^2 \pi}{9} + \frac{V_1^2 \pi}{3} + \frac{V_1^2 \pi}{9} \right)} = \sqrt{\frac{1}{\pi} \left(\frac{5V_1^2 \pi}{9} \right)} \\
 &= \sqrt{5} \frac{V_1}{3} = 0.7453V,
 \end{aligned}$$

The average value is also to be obtained over half cycle

$$\begin{aligned}
 V_{avg} &= \frac{\int_0^{\pi} V(t) dt}{\pi} = \frac{1}{\pi} \left[\int_0^{\frac{\pi}{2}V_3} V_1(t) dt + \int_{\frac{\pi}{2}V_3}^{\frac{3\pi}{2}V_3} V_2(t) dt \right. \\
 &\quad \left. + \int_{\frac{3\pi}{2}V_3}^{\pi} V_3(t) dt \right] \\
 \Rightarrow \int_0^{\frac{\pi}{2}V_3} V_1(t) dt &= \int_0^{\frac{\pi}{2}V_3} \frac{3V_1 t}{\pi} dt = \frac{3V_1}{\pi} \left[\frac{t^2}{2} \right]_0^{\frac{\pi}{2}V_3} = \boxed{\frac{V_1 \pi}{6}} \rightarrow (1)
 \end{aligned}$$


$$\begin{aligned}
 \int_{\frac{\pi}{3}}^{\frac{2\pi}{3}} V(t) dt &= \int_{\frac{\pi}{3}}^{\frac{2\pi}{3}} V_1 dt = V_1 \left(\frac{2\pi}{3} - \frac{\pi}{3} \right) = V_1 \left(\frac{\pi}{3} \right) \rightarrow ① \\
 \int_{\frac{2\pi}{3}}^{\pi} V(t) dt &= \int_{\frac{2\pi}{3}}^{\pi} \left[-\frac{3V_1 t}{\pi} + 3V_1 \right] dt \\
 &= -\frac{3V_1}{\pi} \left[-\frac{t^2}{2\pi} + t \right]_{\frac{2\pi}{3}}^{\pi} \\
 &= 3V_1 \left[\left(-\frac{\pi^2}{2\pi} + \pi \right) - \left(-\frac{4\pi^2}{9 \times 2\pi} + \frac{2\pi}{3} \right) \right] \\
 &= 3V_1 \left[\pi_2 + \frac{8\pi}{9} - \frac{2\pi}{3} \right] = 3V_1 \left[\frac{7\pi + 12\pi}{18} \right] \\
 &= 3V_1 \left[\frac{19\pi}{18} \right] = \boxed{V_1 \frac{\pi}{6}} \rightarrow ②
 \end{aligned}$$

$\therefore V_{avg} = \frac{1}{\pi} [① + ② + ③]$

$$= \frac{1}{\pi} \left[\frac{V_1 \pi}{6} + \frac{V_1 \pi}{3} + \frac{V_1 \pi}{6} \right] = \frac{2V_1}{3} = 0.666V_1$$

$$K_f = \text{form factor} = \frac{\text{R.m.s}}{\text{Avg value}} = \frac{0.7453V_1}{0.666V_1} = 1.1179.$$

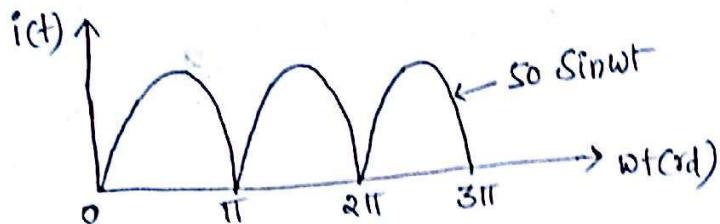Q) The current of the following wave-form is passed through 5 ohms resistor
Find the power consumed?




Sol) Let us find the r.m.s Value of the current,
 $T = \pi$ (Time period)

$$\begin{aligned}
 i(t) &= 50 \sin \omega t \\
 I_{rms} &= \sqrt{\frac{1}{\pi} \int_0^{\pi} i^2(t) d(\omega t)} = \sqrt{\frac{1}{\pi} \int_0^{\pi} 2500 \sin^2 \omega t d(\omega t)} \\
 &= \frac{50}{\sqrt{\pi}} \sqrt{\int_0^{\pi} \sin^2 \omega t d(\omega t)} = \frac{50}{\sqrt{\pi}} \sqrt{\int_0^{\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d(\omega t)}
 \end{aligned}$$


Phase of a Sinewave

7

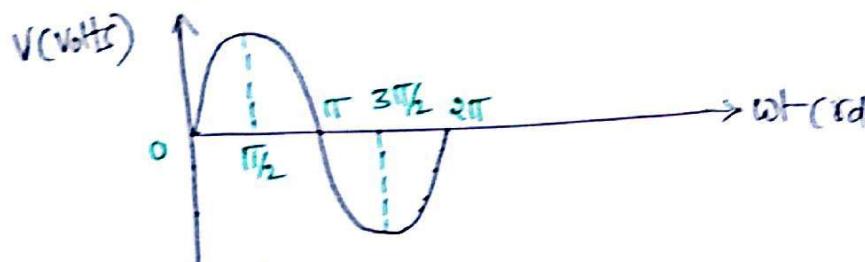The phase of a Sine wave is an angular measurement that specifies the position of the Sine wave relative to a reference.




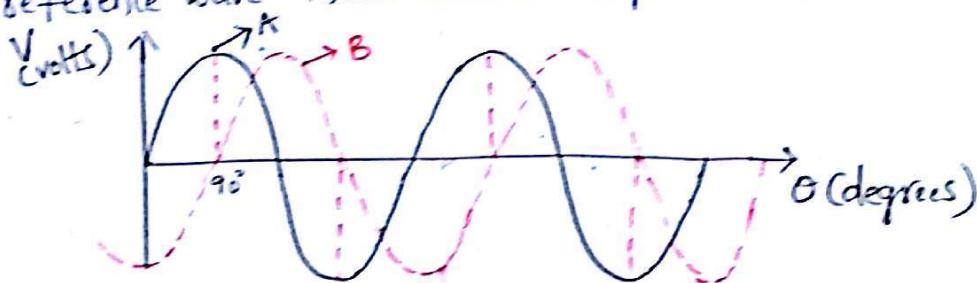When the Sine wave is shifted left (or) right with respect to the Reference wave there occurs a phase shift.



The Sine wave is shifted to the right by 90° ($\pi/2$ rad) shown by the dotted lines. There is a phase angle of 90° between A and B.

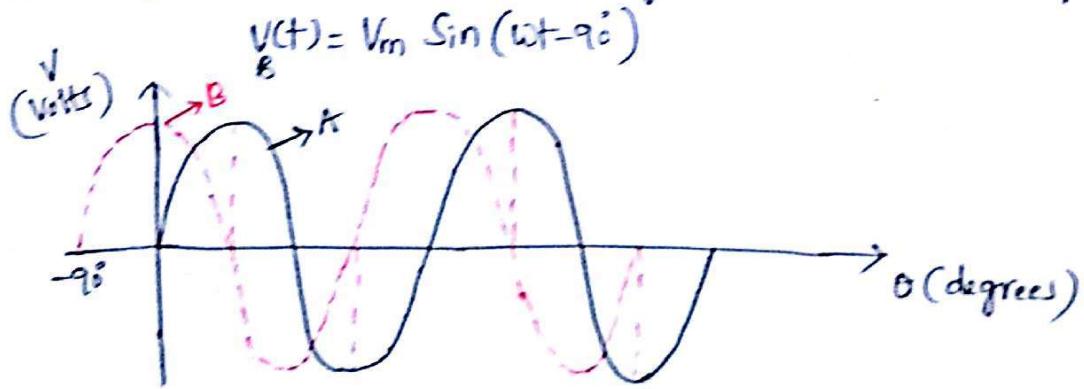Here the waveform B is lagging behind waveform A by 90° . In other words, the Sine wave A is leading the Sine wave B by 90° .



The Sine wave A is lagging behind the waveform B by 90° .


$$V_B(t) = V_m \sin(\omega t + 90^\circ)$$

$$= \frac{50}{\sqrt{2}\pi} \sqrt{\int_0^{\pi} (1 - \cos 2wt) d(wt)} = \frac{50}{\sqrt{2}\pi} \sqrt{\left(wt - \frac{\sin 2wt}{2} \right)_0^{\pi}} \quad (1)$$

$$I_{rms} = \frac{50}{\sqrt{2}\pi} \sqrt{(\pi - 0) - (0)} = \frac{50}{\sqrt{2}\pi} \times \sqrt{\pi} = \frac{50}{\sqrt{2}} = 35.3553 A$$

$$\text{Power consumed by Resistor} = I_{rms} \times R = (35.3553)^2 \times 5 \\ = 6250 W.$$

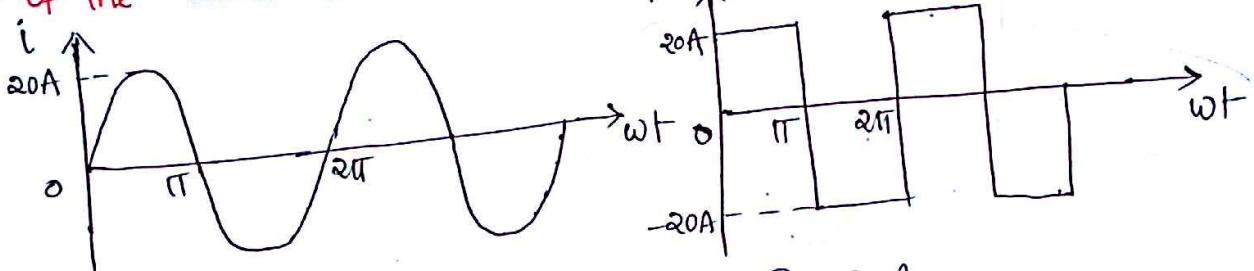7) A resistor carries two alternative currents having same frequency and phase and having the same peak value of 20A. one is sinusoidal and the other is rectangular in waveform. Find the R.m.s value of the resultant current?



Consider Sinusoidal Current with $I_m = 20 A$.

For Sinusoidal current

$$I_{rms-1} = \frac{I_m}{\sqrt{2}} = \frac{20}{\sqrt{2}} = 14.1421 A$$

Consider Rectangular Current with $I_m = 20 A$

$$I_{rms-2} = \sqrt{\frac{1}{\pi} \int_0^{\pi} i^2 d(wt)}$$

$$i = 20$$

$$= \sqrt{\frac{1}{\pi} \int_0^{\pi} (20)^2 d(wt)}$$



$$= \sqrt{\frac{400}{\pi} \left(wt \right)_0^{\pi}} = \frac{20}{\sqrt{\pi}} \sqrt{(\pi - 0)} = \frac{20}{\sqrt{\pi}} \times \sqrt{\pi} \\ = 20$$

\therefore Total R.m.s Current

$$I_{rms} = \sqrt{I_{rms-1}^2 + I_{rms-2}^2}$$

$$= \sqrt{(14.1421)^2 + (20)^2}$$

$$= 24.4948 A$$

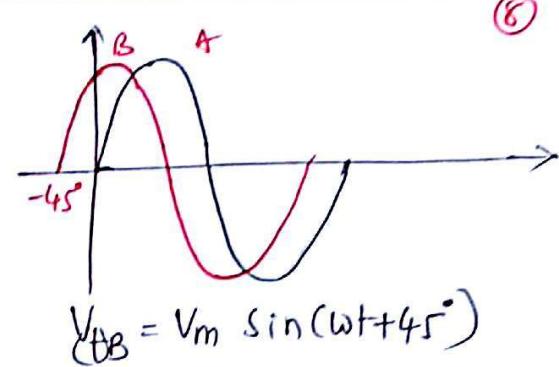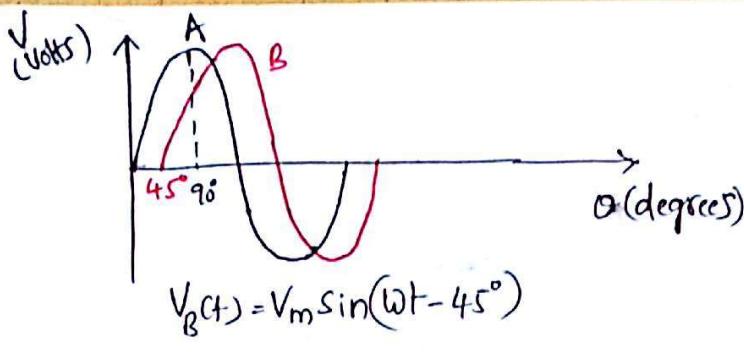

Phasor representation of an alternating quantity

The Sinusoidally Varying alternating quantity can be represented graphically by a straight line with an arrow in the phasor representation method. This is similar to vector such a line is called a phasor.


The phasors are assumed to be rotate in anticlockwise direction with a constant speed $\omega \text{ rad/sec}$.

→ In the analysis of alternating quantities, it is necessary to know the position of the phasor representing that alternating quantity at a particular instant.


→ In general phase ϕ of an alternating quantity varies from $\phi=0$ to $2\pi \text{ rad}$ (or) $\phi=0^\circ$ to 360°

Let $V = V_m \sin(\omega t \pm \phi)$ equation in terms of phasor

$$\phi=0, V=V_m \sin \omega t$$


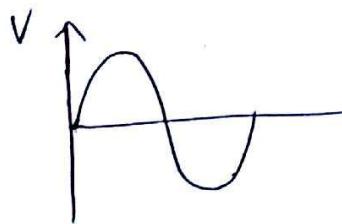


phasor diagram

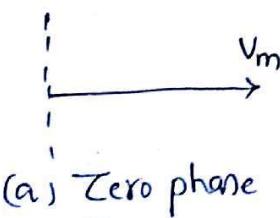



$$\phi = +90^\circ$$

$$V = V_m \sin(\omega t + 90^\circ)$$

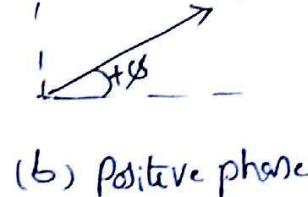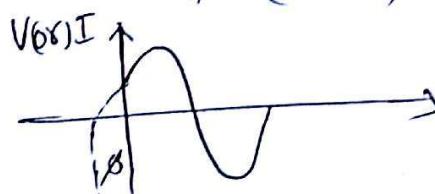

$$\phi = -90^\circ$$

$$V = V_m \sin(\omega t - 90^\circ)$$

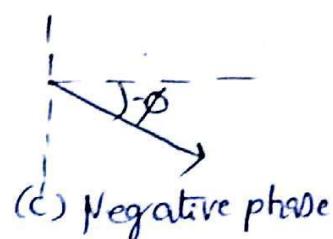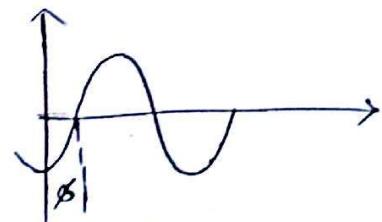

Note :-

1. The phase is measured with respect to reference direction i.e positive x-axis direction.
 2. The phase measured in anti-clockwise direction is positive while the phase measured in clockwise direction is negative.
- The difference between the phases of the two alternating quantities is called the phase difference. which is nothing but the angle difference b/w the two phasors representing the two alternating quantities.


Phasor diagram :- The diagram in which different alternating quantities of the same frequency, sinusoidal in nature are represented by individual phasors indicating exact phase interrelationship is known as phasor diagram.

Q) Two sinusoidal currents are given by $i_1 = 10 \sin(\omega t + \pi/3)$ and $i_2 = 15 \sin(\omega t - \pi/4)$. Calculate the phase difference between them in degrees and draw the phasor diagram?

Given $i_1 = 10 \sin(\omega t + \pi/3)$

$i_2 = 15 \sin(\omega t - \pi/4)$

phasor diagram

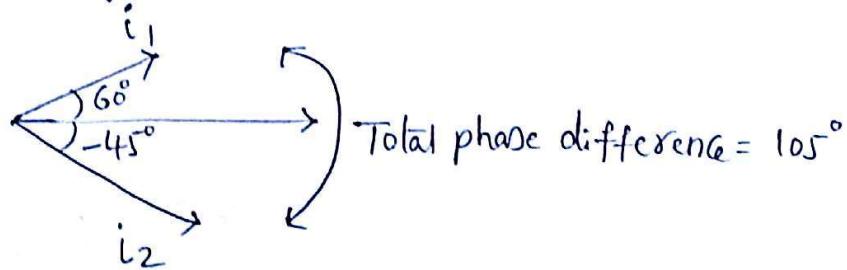

1) zero phase difference :-



Consider two alternating quantities having same frequency $f \text{ Hz}$ and different maximum values

$$V = V_m \sin \omega t$$

$$i = I_m \sin \omega t$$

let $V_m > I_m$

phasor representation

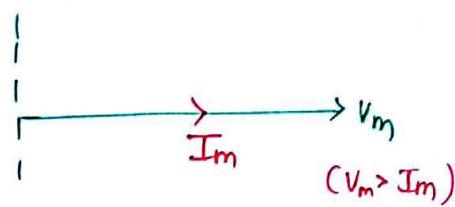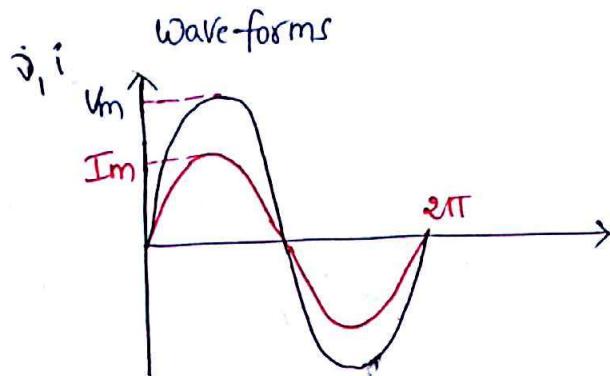

Note: The length of phasor equals to maximum value.


When such phase difference between two alternating quantities is zero, the quantities are said to be in phase.

2) Lagging phase difference:-


let $V = V_m \sin \omega t$ $i = I_m \sin(\omega t - \phi)$ ($V_m > I_m$)

phasor diagram

wave forms

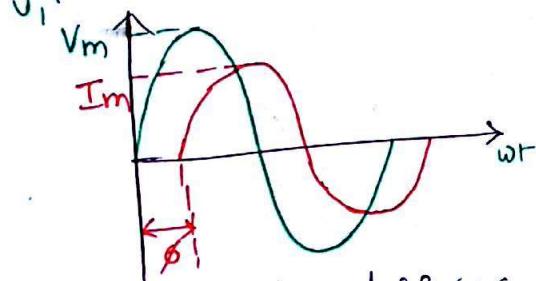

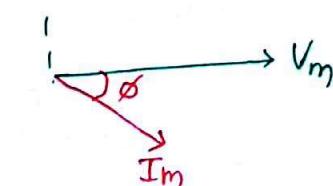There exist a phase difference of ϕ between the two phasors





The current i is said to be lagging with the voltage V by an angle ϕ .

3) Leading phase difference:-

let $V = V_m \sin \omega t$ $i = I_m \sin(\omega t + \phi)$ ($V_m < I_m$)

phasor diagram

wave forms

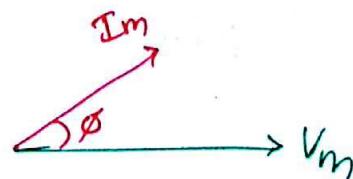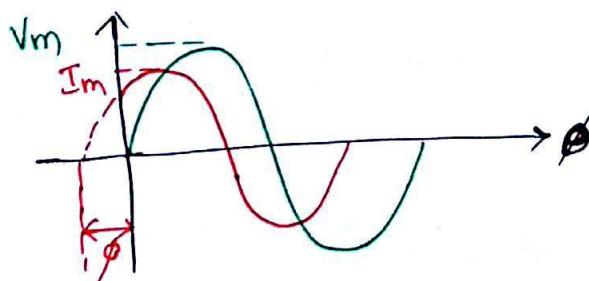

The current i is said to be leading with the voltage V by an angle ϕ .

Mathematical Representation of phasor

The algebraic operations such as addition, subtraction etc with waveforms are more complicated and time consuming. Hence it is necessary to represent the phasors mathematically.

Any phasor can be represented mathematically in two ways.

- 1) polar co-ordinate system.
- 2) Rectangular co-ordinate System.

Polar Co-ordinate system

Consider an alternating current $i = I_m \sin(\omega t + \phi)$

thus its maximum value is I_m and phase is ϕ . The phase ϕ is always measured with respect to X-axis direction.

→ while representing this phasor by polar system, it is represented as $\gamma \angle \phi$

where $\gamma = \frac{I_m}{\sqrt{2}}$ (RMS Value)

ϕ = phase angle with respect to +ve X-axis



Polar form

→ So draw a line at an angle ϕ measured w.r.t +ve X-axis from the origin and measure a distance equal to $\gamma = \frac{I_m}{\sqrt{2}}$

Polar representation of phasor mathematically


$$= \gamma \angle \phi$$

Q) Represent $V = 40 \sin(\omega t + 11\frac{1}{3})$ in polar coordinate system?

Given - $V = 40 \sin(\omega t + 11\frac{1}{3})$

Polar form $\gamma \angle \phi$
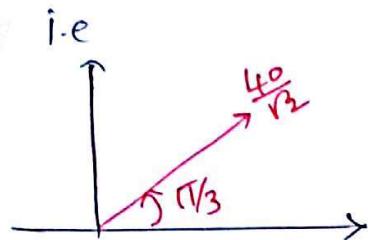
$$\gamma = \frac{40}{\sqrt{2}} \quad \phi = +11\frac{1}{3} \quad \therefore \text{Polar form} = \frac{40}{\sqrt{2}} \angle +11\frac{1}{3}$$




2). Rectangular Co-ordinate System:-

Mathematically an alternating quantity can be divided into two components, X-component and Y-component.

$$\text{If } i = I_m \sin(\omega t + \phi)$$

$$X\text{-component} = I_m \cos\phi$$

$$Y\text{-Component} = I_m \sin\phi$$

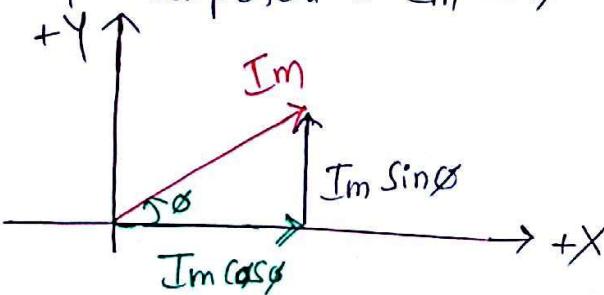

→ X and Y-Components can be +Ve (or) -Ve

→ To indicate that X and Y components are perpendicular to each other, The operator 'j' is used in mathematical representation of phasor in rectangular co-ordinate system.

Mathematical representation of rectangular co-ordinate system

$$= \pm x \pm jy$$

Mathematically Value of $j = \sqrt{-1}$

but in the phasor representation $j = 1 (90^\circ)$

i.e. rotation through 90°

10) Represent $i = 20 \sin(\omega t + \pi/6)$ in rectangular co-ordinate system?

$$\text{Given } i = 20 \sin(\omega t + \pi/6)$$

$$I_m = 20 \quad \text{and} \quad \phi = \pi/6$$

$$X\text{-component} = I_m \cos\phi = 20 \times (\sqrt{3}/2) = 10\sqrt{3}$$

$$Y\text{-Component} = I_m \sin\phi = 20 \times (\sqrt{3}/2) = 10\sqrt{3}$$


Then $i = 20 \sin(\omega t + \pi/6)$ in rectangular co-ordinate system

is $X + jY$

i.e. $10\sqrt{3} + j10$

Polar to Rectangular Conversion

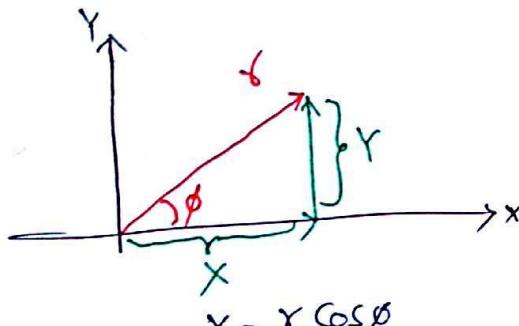
Polar form for phasor is $\gamma L\phi$
polar to Rectangular means find X and Y in terms of γ and ϕ



Rectangular to polar conversion :-

Rectangular form of phasor is $X + jY$

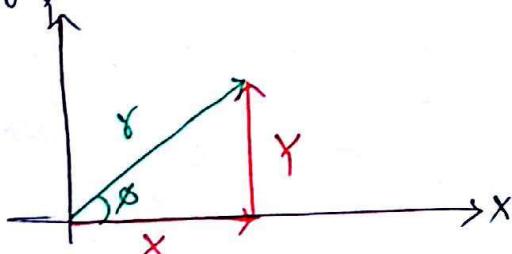Rectangular to polar means find γ and ϕ in terms of X and Y



Find γ and ϕ in terms of X and Y

From diagram $\gamma = \sqrt{X^2 + Y^2}$ $\phi = \tan^{-1}\left(\frac{Y}{X}\right)$

\therefore Polar representation $= \gamma L\phi = \sqrt{X^2 + Y^2} \ L \tan^{-1}\left(\frac{Y}{X}\right)$

Note: - polar form always gives r.m.s value of an alternating quantity.

ii) write polar form of the Voltage given by $v = 100 \sin(100\pi t + \pi/6)$ and also obtain its rectangular form?

$$V_m = 100 \text{ and } \phi = \pi/6 = 30^\circ$$

$$\therefore V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.7106 \text{ V.}$$

11) In polar form = $70.7106 \angle 180^\circ$

(11)

Rectangular form = $X + jY$
= $8 \cos \phi + j 8 \sin \phi$

$$= 61.2371 + j 35.3553 \text{ V}$$

12) Find rms value and phase of the current $I = 25 + j40 \text{ A}$?

Sol: Converts Rectangular to polar form

$$= 8(\phi) = \text{Rms } I\phi$$

$$8 = I_{\text{rms}} = \sqrt{25^2 + 40^2} = 47.699$$

$$\phi = \tan^{-1}\left(\frac{Y}{X}\right) = \tan^{-1}\left(\frac{40}{25}\right) = 57.99$$

$$I = 47.699 \angle 57.99^\circ$$

13) A voltage is defined as $-V_m \cos \omega t$. Express it in polar form?

$$V = -V_m \cos \omega t$$

$$\begin{aligned} \sin(90^\circ + \phi) &= \cos \phi \\ \sin(180^\circ + \phi) &= -\sin \phi \end{aligned}$$

$$= -V_m \sin(\omega t + \pi/2)$$

$$= V_m \sin(\omega t + \pi + \pi/2)$$

$$= V_m \sin(\omega t + 3\pi/2)$$

$$\therefore \text{In polar form } V = \frac{V_m}{\sqrt{2}} \angle -3\pi/2$$

(or)

$$V = \frac{V_m}{\sqrt{2}} \angle -90^\circ$$

Note:- 1. For addition and subtraction of alternating quantities use rectangular form of representation of phasors

2. For multiplication and division use polar form of representation of phasors.

14) Three voltages represented by $V_1 = 20 \sin \omega t$, $V_2 = 30 \sin(\omega t - \pi/4)$ and $V_3 = 40 \cos(\omega t + \pi/6)$ act together in a circuit. Find expression for the resultant voltage?

In polar form

$$V_1 = \frac{20}{\sqrt{2}} \angle 0^\circ = 14.1421 \angle 0^\circ$$

$$V_2 = \frac{30}{\sqrt{2}} \angle -45^\circ = 21.2132 \angle -45^\circ$$


$$V_3 = 40 \cos(\omega t + \pi/6) = 40 \sin(90^\circ + \omega t + 30^\circ) = 40 \sin(\omega t + 120^\circ)$$

$$V_R = \frac{I_0}{\sqrt{R}} (1 - e^{-\frac{t}{RC}}) = 28.4848 \text{ V}$$

$$\therefore V_R = V_1 + V_2 + V_3 = 181.594948 + 17.95841393 \text{ V}$$

A.C. Through pure Resistance, Inductance and Capacitance

1) A.C. through pure Resistance :-

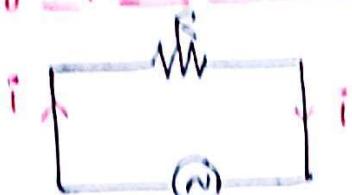



According to Ohm's law
 $V = V_m \sin \omega t$

$$i = \frac{V}{R} = \frac{V_m \sin \omega t}{R} = \left(\frac{V_m}{R}\right) \sin \omega t$$

$$\therefore I_m = \frac{V_m}{R}$$


$\phi = 0$

phasor diagram

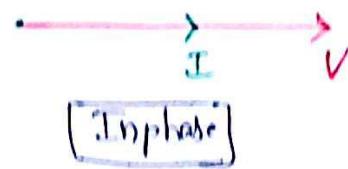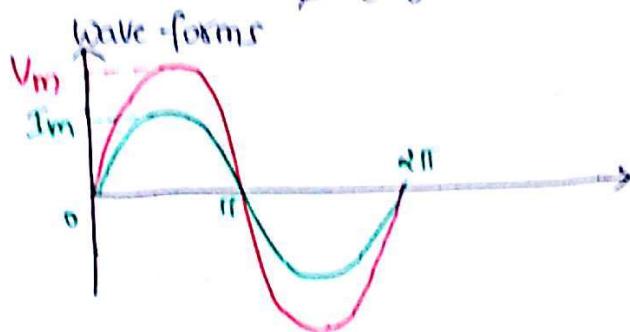

In purely resistive circuit, the current and voltage applied are inphase with each other.

2) A.C. through pure Inductance :-

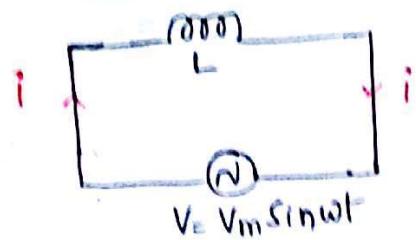

The current flowing through the inductor

$$i = \frac{1}{L} \int v dt = \frac{1}{L} \int V_m \sin \omega t dt$$

$$= \frac{V_m}{L} \left(-\frac{\cos \omega t}{\omega} \right) = \frac{V_m}{L \omega} \sin \left(\frac{\pi}{2} - \omega t \right)$$

$$i = -\frac{V_m}{L\omega} \cos \omega t = -\frac{V_m}{L\omega} \sin(\pi/2 - \omega t)$$

(12) $\therefore \sin(90^\circ - \theta) = \sin \theta$

$$i = \frac{V_m}{L\omega} \sin(\omega t - \pi/2)$$

$$i = \frac{V_m}{X_L} \sin(\omega t - \pi/2)$$

$X_L = L\omega$ = Inductive Reactance.



$$i = I_m \sin(\omega t - \pi/2)$$

The above equation purely shows that the current is sinusoidal and having phase angle of $-\pi/2$ radians. i.e. 90° . This means that the current lags Voltage applied by 90° .

→ The negative sign indicates lagging nature of the current.

waveforms

phasor diagram

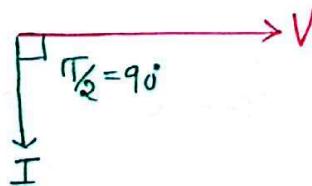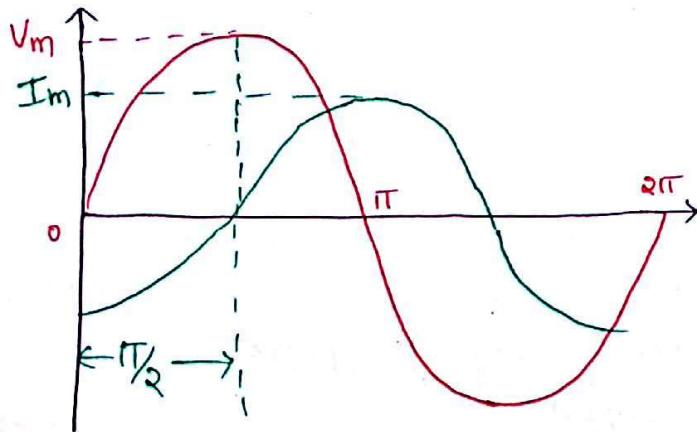

In purely inductive circuit, Current lags Voltage by 90° .

Inductive Reactance :- ($X_L = L\omega$)

The inductive reactance is defined as the opposition offered by the inductance of a circuit to the flow of an alternating current.

$$X_L = L\omega = L 2\pi f \Omega$$


It is measured in ohms.

Power :-

The expression for the instantaneous power can be obtained by taking the product of instantaneous Voltage and Current.

$$\begin{aligned}
 P &= V \times i = V_m \sin \omega t \times I_m \sin(\omega t - \frac{\pi}{2}) \\
 &= V_m \sin \omega t \times I_m - \sin(\frac{\pi}{2} - \omega t) \\
 &= -V_m I_m \sin \omega t \cos(\omega t) \\
 &= -\frac{V_m I_m}{2} \sin(2\omega t). \text{ (double the frequency of voltage)}
 \end{aligned}$$


avg power taken by Inductor

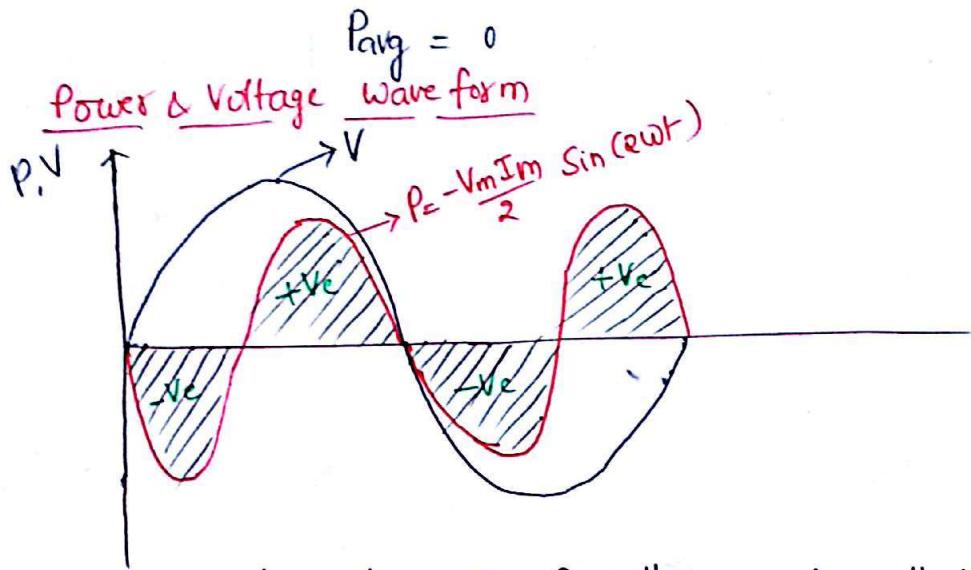

It can be observed from the wave-form that * power curve is positive, energy gets stored in the magnetic field established due to the increasing current while during negative power curve, this power is returned back to the supply.

* pure inductance never consumes power.

A.C through Pure Capacitance :

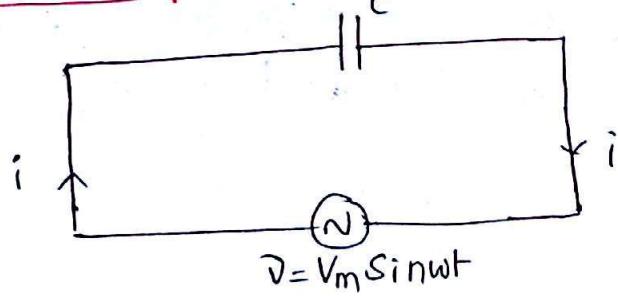

The current flowing through the capacitance is

$$i = C \frac{dv}{dt} = C \frac{d}{dt} [V_m \sin \omega t] = CV_m \cos \omega t \cdot \omega$$


$$i = V_m \omega \cos \omega t = \frac{V_m}{(Y_C \omega)} \cos \omega t.$$

$$i = \frac{V_m}{X_c} \cos \omega t = \frac{V_m}{X_c} \sin(\pi/2 + \omega t) \quad (13) \quad \sin(\theta_0 + \omega) \\ = \cos \theta$$

$$X_c = \text{Capacitive Reactance} = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$


$$\therefore i = \frac{V_m}{X_c} \sin(\omega t + \pi/2)$$

$$i = I_m \sin(\omega t + \pi/2)$$

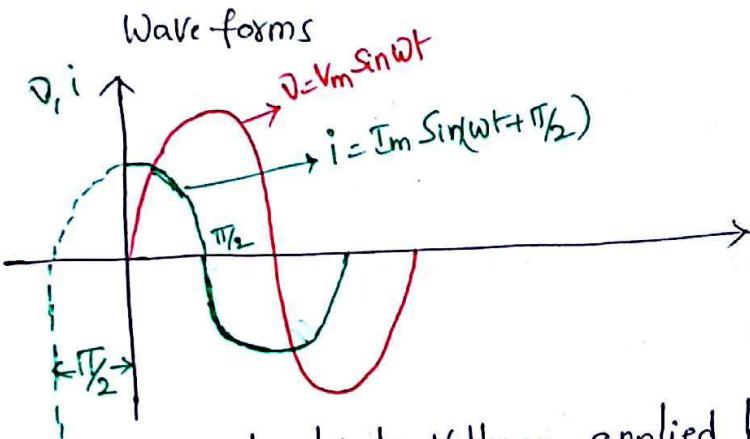

Current leads Voltage applied by 90° . The positive sign indicates leading nature of the current.

Phasor diagram

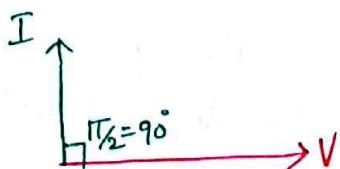

Power :-

The expression for the instantaneous power can be obtained by taking the product of instantaneous Voltage and current.

$$P = V_i = V_m \sin \omega t \times I_m \sin(\omega t + \pi/2)$$

$$= \frac{V_m I_m}{2} \sin \omega t \cos \omega t$$


$$= \frac{V_m I_m}{2} \sin 2\omega t$$

Power curve is a sine wave of frequency double that of applied voltage.

→ The average value of Sine curve over a complete cycle is always zero.

$$P_{av} = 0$$

Hence average power consumption is zero.

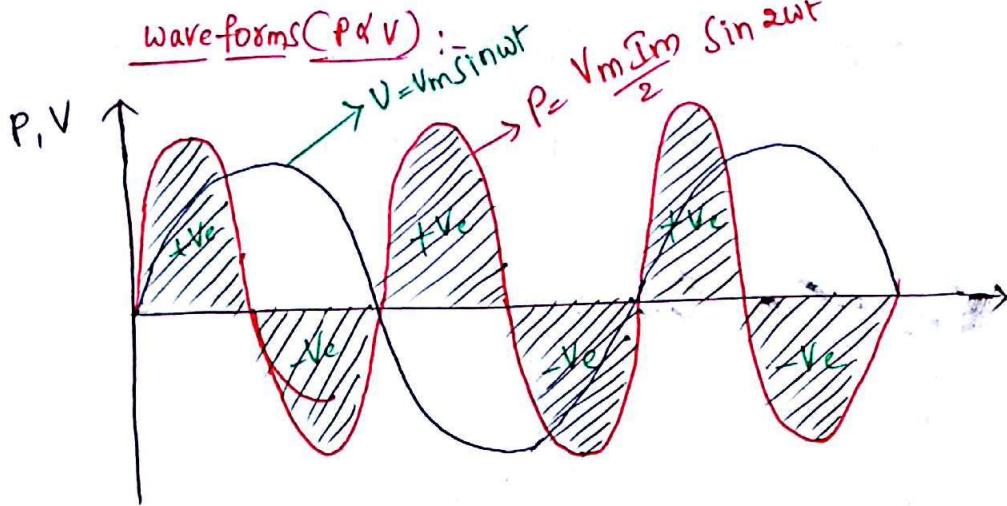


Impedance :-

The opposition offered by an electric circuit to the flow of an alternating current is called an impedance. It is denoted by Z .

It is defined as the ratio of an alternating Voltage to an alternating current through the circuit.

Impedance is complex and is expressed in polar (or) rectangular form.

For Resistance :-

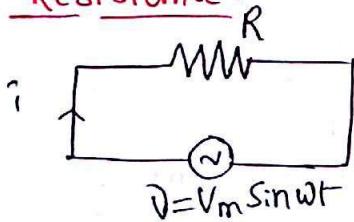

$$V = V_m \sin \omega t$$


$$i = I_m \sin \omega t = \frac{V_m}{R} \sin \omega t$$

$$\therefore Z = \frac{V}{i} = \frac{V_m \sin \omega t}{\frac{V_m}{R} \sin \omega t} = R$$

in Rectangular form $Z = R + j0$

polar form $Z = R \angle 0^\circ$

For pure Inductance :-

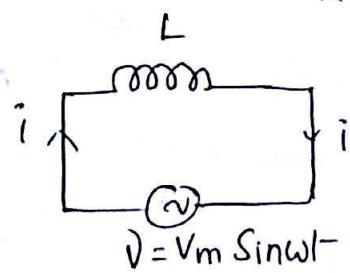

$$V = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - \pi/2)$$

$$= \frac{V_m}{L \omega} \sin(\omega t - \pi/2)$$

In polar form $V = \frac{V_m}{L \omega} \angle -90^\circ$

$$Z = \frac{V_m}{I_m} \angle -90^\circ$$


$$i = \frac{V_m}{\sqrt{2} L \omega} \angle -45^\circ$$

$$Z = \frac{V}{I} = \frac{\frac{V_m}{\sqrt{2}} \text{ } L^{\circ}}{\frac{V_m}{\sqrt{2}} \text{ } L^{\circ} \text{ } \left[-\frac{\pi}{2} \right]} = L \omega \text{ } \left[\text{IV}_2 \right] = jL\omega$$

(14)

$$\therefore Z = jL\omega = jX_L$$

For pure capacitance :-

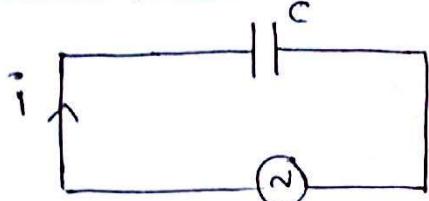

$$V = V_m \sin \omega t$$

$$\text{In polar form } V = \frac{V_m}{\sqrt{2}} L^{\circ}$$


$$i = \frac{V_m}{\sqrt{2} X_C} \left(\frac{\pi}{2} \right)$$

$$\therefore Z = \frac{V}{I} = \frac{\frac{V_m}{\sqrt{2}} L^{\circ}}{\frac{V_m}{\sqrt{2} X_C} \left(\frac{\pi}{2} \right)} = X_C \left[-\frac{\pi}{2} \right] = -jX_C$$

$$-j = 1 \left[-\frac{\pi}{2} \right]$$



$$\therefore Z = -jX_C$$

Series Circuits

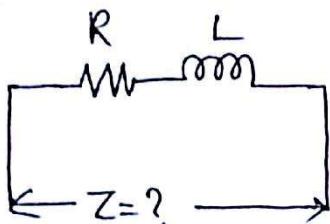



$$Z = R + jX_L$$

Impedance triangle

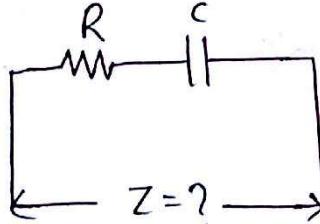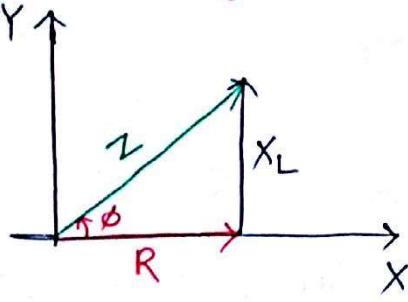


$$Z = R - jX_C$$

Impedance Triangle

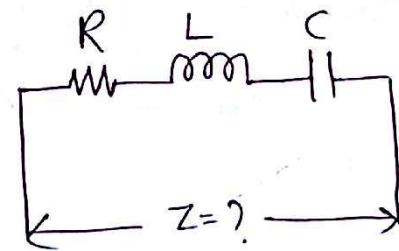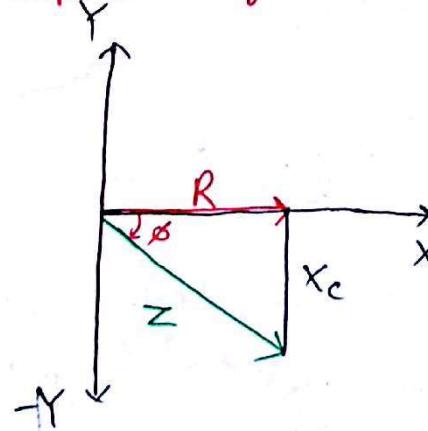

$$Z = R + jX_L - jX_C$$

Impedance Triangle

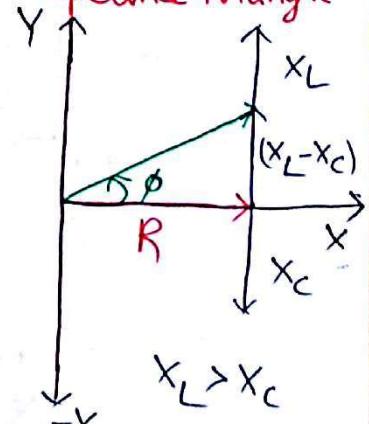

Polar form

$$Z = R + jX_L$$

$$Z = \sqrt{R^2 + X_L^2} \left[\tan^{-1} \left(\frac{X_L}{R} \right) \right] \\ = Z \angle \phi$$

Polar form

$$Z = R - jX_C$$


$$Z = \sqrt{R^2 + X_C^2} \left[-\tan^{-1} \left(\frac{X_C}{R} \right) \right] \\ = Z \angle -\phi$$

Polar form

$$Z = R + j(X_L - X_C)$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \left[\tan^{-1} \left(\frac{X_L - X_C}{R} \right) \right] \\ = Z \angle \theta$$

1. Series RL Circuit :-

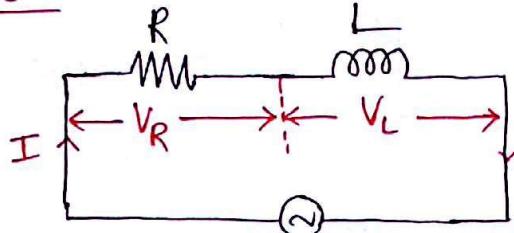

where

$$V_R = \text{Drop across pure resistance} = I \times R$$

$$V = V_m \sin \omega t$$

$$V_L = \text{Drop across pure Inductance} = I \times X_L$$

$$\text{Impedance } Z = R + jX_L$$

$$Z = \frac{V}{I}$$

$$V = IZ = I(R + jX_L)$$



$$V = IR + jIX_L$$

$$\boxed{\bar{V} = \bar{V}_R + \bar{V}_L} \quad (\text{From K.V.L})$$

Note:- In series circuit take current as reference in phasor diagram.

phasor diagram :-

Voltage Triangle

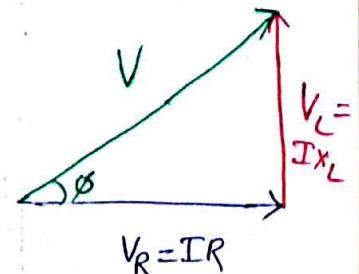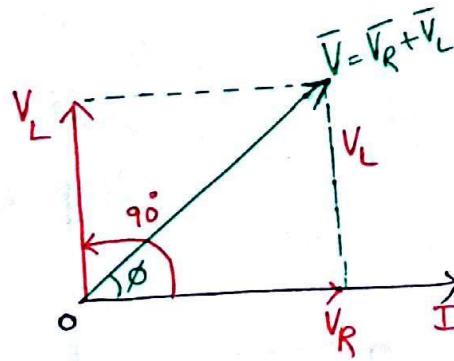

It can be observed that- Current lags Voltage by angle ϕ

$$V(t) = V_m \sin \omega t \quad i(t) = I_m \sin(\omega t - \phi)$$

$$\phi = \tan^{-1} \left(\frac{V_L}{V_R} \right) = \tan^{-1} \left(\frac{I X_L}{I R} \right) = \tan^{-1} \left(\frac{X_L}{R} \right)$$

(15)

Power and Power triangle:-

The expression for the current in the series R-L circuit is,
 $i = I_m \sin(\omega t - \phi)$ as current lags voltage.

The instantaneous power is given by

$$\begin{aligned} P &= V \times i = V_m \sin \omega t \times I_m \sin(\omega t - \phi) \\ &= V_m I_m [\sin(\omega t) \cdot \sin(\omega t - \phi)] \\ &= V_m I_m \left[\frac{\cos(\phi) - \cos(2\omega t - \phi)}{2} \right] = \frac{V_m I_m}{2} \cos \phi - \\ &\quad \frac{V_m I_m}{2} \cos(2\omega t - \phi) \end{aligned}$$

$$\left(\because 2 \sin A \sin B = \cos(A-B) - \cos(A+B) \right)$$

Now, the second term is cosine term whose average value over a cycle is zero. Hence average power consumed is,

$$P_{av} = \frac{V_m I_m}{2} \cos \phi = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi$$

$$P_{av} = V I \cos \phi$$

where V and I are r.m.s values

In Series RL circuit

$$\bar{V} = \bar{V}_R + \bar{V}_L$$

Multiply voltage equation by current I, Then we get

The expression for total power input i.e

$$\bar{V}I = \bar{V}_R I + \bar{V}_L I$$


From Voltage triangle

$$V_R = V \cos \phi$$

$$V_L = V \sin \phi$$

$$\bar{V}I = \overline{V \cos \phi I} + \overline{V \sin \phi I}$$

Power triangle

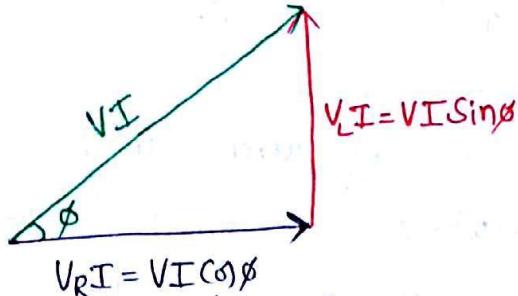

So three sides of this triangle are

- 1) VI
- 2) $VI \cos \phi$
- 3) $VI \sin \phi$

1. Apparent power (S) :-

It is defined as the product of r.m.s Value of Voltage (V) and current (I). It is denoted by S.

$$S = VI \quad VA$$

It is measured in unit Volt-ampere (VA) (or) KVA

2. Real (or) True power (P) :-

If means the useful power from the source to the load, which is also called true power.

It is defined as the product of the effective values of both voltage and current multiplied by cosine of the phase angle between voltage and the current.

It is measured in watts (W), (or) kW

$$P = VI \cos \phi \quad \text{watts.}$$

3. Reactive power (Q) :-

It is defined as the product of the r.m.s Values of both voltage and current multiplied by Sine of the phase angle between voltage and the current

→ It is also defined as imaginary component of the apparent power. It is represented by 'Q' and it is measured in Volt-amp reactive (VAR) (or) kVAR

$$Q = VI \sin \phi \quad \text{VAR}$$

Power factor ($\cos\phi$):-

It is defined as the ratio of true power to apparent power
(or)

It is defined as the cosine of phase angle between Voltage and Current.

$$\text{Power factor } (\cos\phi) = \frac{\text{True Power}}{\text{Apparent power}} = \frac{VI \cos\phi}{VI} = \cos\phi$$

→ As the phase angle between Voltage and total current increases, the power factor decreases. The smaller the power-factor, the smaller the power dissipation. The power-factor varies from 0 to 1.

→ It is also defined as the ratio of resistance to the impedance
(from impedance triangle)

$$\cos\phi = \frac{R}{Z}$$

→ Note:- The nature of power-factor is always determined by position of current with respect to the Voltage.

→ If Current lags Voltage, power-factor is said to be lagging power factor

→ If current leads Voltage, power-factor is said to be leading power-factor

→ If current is inphase with Voltage, power-factor is said to be unity power factor.

For pure Resistive :-

$$\phi = 0, \cos\phi = \cos(0) = 1 \quad \text{unity power factor}$$

For pure Inductive :-


$$\phi = \pi/2 \text{ lag.} \cos(\pi/2) = 0 \quad \text{Zero lagging power factor}$$

For pure Capacitive :-

$$\phi = \pi/2 \text{ lead} \quad \cos(\pi/2) = 0 \quad \text{Zero leading power factor.}$$

A 20Ω resistance and 30 mH inductance are connected in series and the circuit is fed from a $230\text{V}, 50\text{Hz}$ AC Supply. Find

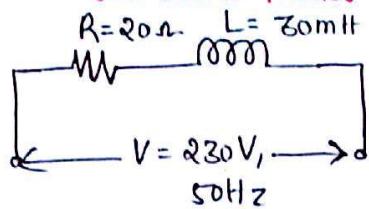- Reactance across the inductance, impedance, admittance, current
- Voltage across Resistance (iii) Voltage across the inductance
- Real, reactive and active powers (v) Power factor.



$$(i) X_L = L\omega = L \times 2\pi f$$

$$= 30 \times 10^{-3} \times 2\pi \times 50 = 9.4248 \Omega$$

$$Z = R + jX_L = 20 + j9.4248 \Omega$$

$$= 22.1094 \angle 25.2317^\circ \Omega$$

$$\text{admittance } Y = \frac{1}{Z} = \frac{1}{22.1094 \angle 25.2317^\circ} = 0.04522 \angle -25.2317^\circ \text{ S}$$

$$I = \frac{V}{Z} = \frac{230 \angle 0^\circ}{22.1094 \angle 25.2317^\circ} = 10.4028 \angle -25.2317^\circ \text{ A}$$

$$(ii) V_R = IR = (10.4028 \angle -25.2317^\circ) \times 20 \angle 0^\circ = 208.056 \angle -25.2317^\circ \text{ V}$$

$$(iii) V_L = I \times jX_L = 10.4028 \angle -25.2317^\circ \times j9.4248$$

$$= 98.0443 \angle 64.7683^\circ \text{ V}$$

$$(iv) P = VI \cos\phi = 230 \times 10.4028 \times \cos(-25.2317^\circ) = 2164.365 \text{ W}$$

$$Q = VI \sin\phi = 230 \times 10.4028 \times \sin(-25.2317^\circ) = -1019.9359 \text{ VAR}$$

The negative sign indicates lagging nature of reactive Volt-ampere.

$$S = VI = 230 \times 10.4028 = 2392.644 \text{ VA}$$

$$(v) \text{ Power factor} = \cos\phi = \cos(-25.2317^\circ) = 0.90459 \text{ lagging}$$

A Series Circuit with a resistance $R = 10\Omega$ and inductance 20mH has a current of $i = 2 \sin 500t$. obtain the total voltage across the series circuit and angle by which the current lags the voltage?

$$i(t) = 2 \sin 500t$$

$$\omega = 500 \text{ rad/sec}$$


$$2\pi f = 500, f = \frac{500}{2\pi} =$$

(17)

$$X_L = L\omega = 500 \times 20 \times 10^{-3} = 10 \Omega$$

$$Z = R + jX_L = 10 + j10 \Omega$$

$$= 14.1421 \angle 45^\circ \Omega$$

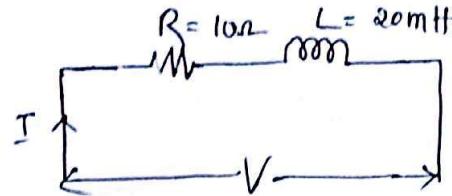

The phase of the current is 0° , i.e. $I = 1.4142 \angle 0^\circ \text{ A}$

$$V = I \times Z = 1.4142 \angle 0^\circ \times 14.1421 \angle 45^\circ = 20 \angle 45^\circ \text{ V}$$


Current lags Voltage by 45°

Series R-C Circuit :-

$$Z = R - jX_C$$

$$V_R = I \times R$$

$$V_C = I \times (-jX_C)$$

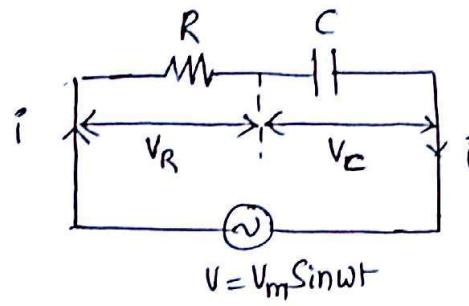



From K.V.L

$$\bar{V} = \bar{V}_R + \bar{V}_C = I \times R + I(-jX_C)$$

$$V = IZ = I(R - jX_C)$$

Phasor diagram :-

Voltage Triangle

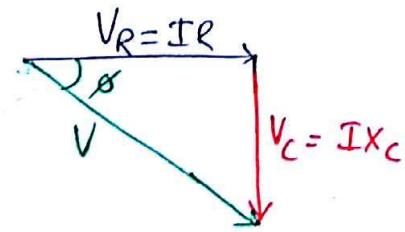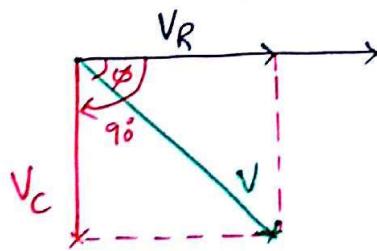

ϕ is the phase angle between voltage (V) and current (I)

It can be seen that current leads voltage by angle ϕ hence

$$V(t) = V_m \sin \omega t \quad I(t) = I_m \sin(\omega t + \phi)$$

Power and Power angle

The current leads Voltage by angle ϕ , hence its expression is,

$$i = I_m \sin(\omega t + \phi)$$

$$P = V \times i = V_m \sin \omega t \times I_m \sin(\omega t + \phi)$$

$$= V_m I_m [\sin \omega t \cdot \sin(\omega t + \phi)] = V_m I_m \left[\frac{\cos(-\phi) - \cos(2\omega t + \phi)}{2} \right]$$
$$= \frac{V_m I_m}{2} \cos \phi - \frac{V_m I_m}{2} \cos(2\omega t + \phi).$$

Now, second term is cosine term whose average value over a cycle is zero. Hence average power consumed by the circuit is,

$$P_{av} = \frac{V_m I_m}{2} \cos \phi = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi$$

$$\boxed{P = VI \cos \phi \text{ Watts.}}$$

In Series RC circuit

$$\bar{V} = \bar{V}_R + \bar{V}_C$$

Multiply Voltage equation by Current I

$$\bar{VI} = \bar{V}_R I + \bar{V}_C I$$


From Voltage triangle

$$V_R = V \cos \phi$$

$$V_C = V \sin \phi$$

$$VI = \underline{V \cos \phi I} + \underline{V \sin \phi I}$$

Power triangle

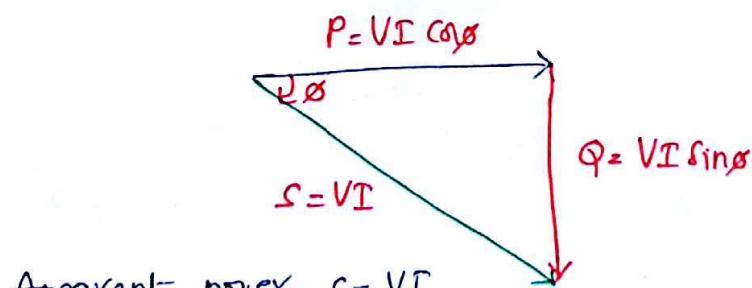

$$\text{Apparent power } S = VI$$

$$\text{True (or) average power } P = VI \cos \phi \text{ W}$$


$$\text{Reactive power } Q = VI \sin \phi \text{ VAR}$$

$$\text{Power factor} = \cos \phi \text{ leading}$$

A Capacitor having a capacitance of $10\ \mu F$ is connected in series with a resistance of 120Ω across 100V , 50Hz . Calculate the power, current and the phase difference between Current and Voltage? (Q8)

Sol
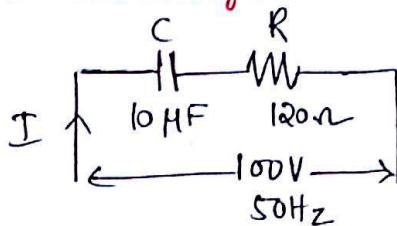
$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 10 \times 10^{-6}} \\ = 318.3098 \Omega$$



$$Z = R - jX_C = (120 - j318.3098)\Omega = 340.178 \angle -69.344^\circ \Omega$$

$$I = \frac{V}{Z} = \frac{100 \angle 0^\circ}{340.178 \angle -69.344^\circ} = 0.2939 \angle 69.344^\circ \text{ A}$$

Phase difference between Voltage and Current = $\phi = 69.344^\circ$ leading

$$P = VI \cos \phi = 100 \times 0.2939 \times \cos(69.344^\circ) = 10.3697 \text{ W.}$$

$$(Q8) P = I^2 R = (0.2939)^2 \times 120 = 10.369 \text{ W.}$$


Series R-L-C Circuit

$$Z = R + j(X_L - X_C)$$

$$V_R = IX_R$$

$$V_L = IX(jX_L)$$

$$V_C = IX(-jX_C)$$

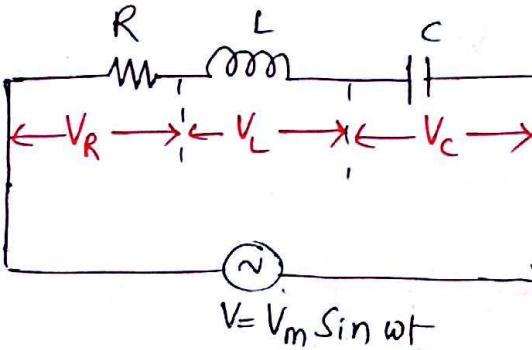


From $I \cdot V \cdot L$

$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$


$$\bar{V} = I(R + j(X_L - X_C))$$

Phasor diagram

Case: 1 $X_L > X_C$ i.e. $V_L > V_C$

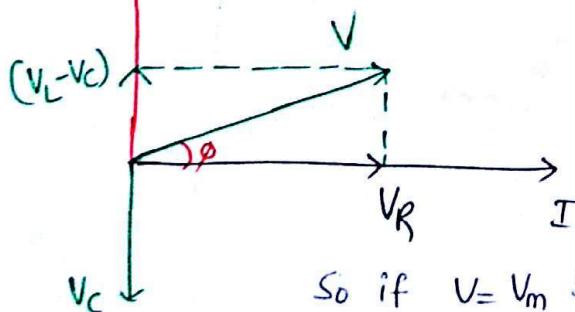



Voltage triangle

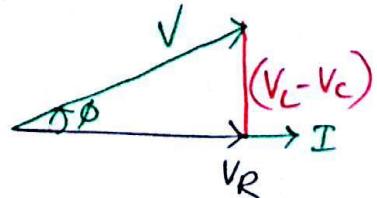

So if $V = V_m \sin \omega t$ then $i = I_m \sin(\omega t - \phi)$


as Current lags Voltage by angle ϕ for $X_L > X_C$.

Case 2: $X_C > X_L$ $V_c > V_L$

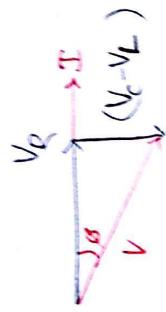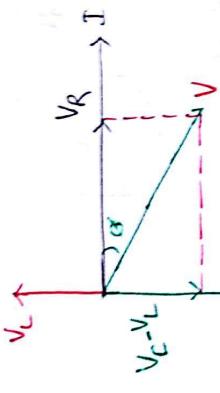

So if $V = V_m \sin(\omega t)$, $\bar{V} = \bar{V}_m \sin(\omega t - \phi)$ as current leads voltage by angle ϕ for $X_C > X_L$.

Case 3: $X_L = X_C$, $V_L = -V_C$

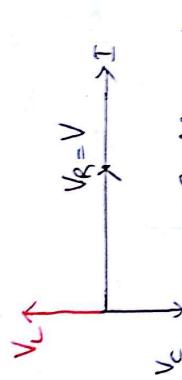


So if $V = V_m \sin(\omega t)$, $\bar{V} = \bar{V}_m \sin(\omega t + \phi)$ as current lags voltage by angle ϕ for $X_L = X_C$.


Power and Power Triangle:

$$P = VI \cos \phi \text{瓦 (for any AC)}$$

Power triangle

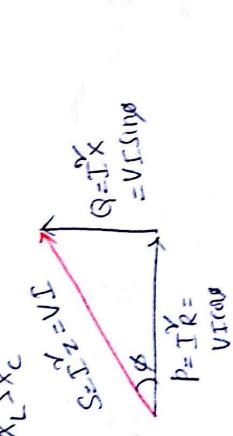

$X_L < X_C$

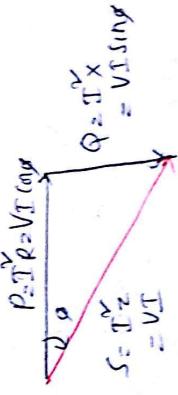

A coil having a resistance of 10 ohms and an inductance of 0.2H is connected in series with a 100×10^{-6} F capacitor across a 230V, 50Hz supply. Calculate.

(19)

(i) The active and reactive components of the current

(ii) The voltage across the coil, draw the phasor diagram

$$X_L = 2\pi fL \\ = 2\pi \times 50 \times 0.2 \\ = 62.8318 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.8309 \Omega$$

$$Z_{coil} = R + jX_L = 10 + j62.8318 \Omega \\ = 63.6226 \angle 80.957^\circ \Omega$$

$$Z_T = Z_{coil} - jX_C = 10 + j62.8316 - j31.8309 \\ = 10 + j31 \Omega = 32.573 \angle 72.121^\circ \Omega$$

$$I = \frac{V}{Z_T} = \frac{230 \angle 0^\circ}{32.573 \angle 72.121^\circ} = 7.061 \angle -72.121^\circ A$$

$$\phi_T = 72.121^\circ \text{ lagging}$$

$$\text{Active Component of Current} = I \cos \phi_T = 7.061 \times 0.307$$

$$\text{Reactive Component of Current} = I \sin \phi_T = 7.061 \times 0.9517$$

$$V_{coil} = I \times Z_{coil} \\ = 7.061 \angle -72.121^\circ \times 63.6226 \angle 80.957^\circ \\ = 449.2391 \angle 8.836^\circ V$$

phasor diagram

